

EE/CSC 327, Laboratory Assignment 2

Name: Shyang Kao

Course name: CSC 327

Due date: February 12, 2022

Experiment Description

Given the following truth table,

<i>a</i>	<i>b</i>	<i>c</i>	<i>F</i>
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

- Find the **Minterm** expansion of the truth table and design the corresponding circuit in Quartus II. Simulate your design and verify that it functions properly according to the truth table.
- Once you are satisfied with your design, download your design in the DE2-115 board and verify that your circuit functions according to the truth table.
For inputs use **SW2**, **SW1** and **SW0** as **a**, **b**, and **c** respectively. For output **F**, use **LEDG1** (** use DE2-115 user manual to do the necessary pin assignment for this design)
- Find the **Maxterm** expansion of the truth table and design the corresponding circuit in Quartus II. Simulate your design and verify that it functions properly according to the truth table.
- Once you are satisfied with your design, download your design in the DE2-115 board and verify that your circuit functions according to the truth table.
For inputs use **SW5**, **SW4** and **SW3** as **a**, **b**, and **c** respectively. For output **F**, use **LEDG2** (** use DE2-115 user manual to do the necessary pin assignment for this design)
- Show that the circuit designed in part (a) can be simplified to a circuit consisting of three NOT gates, two 2-input AND gate and one 2-input OR gate. Draw and simulate your circuit in Quartus II and show that it functions properly according to the truth table.
- Once you are satisfied your design, download the circuit on the DE2-115 board and verify that your circuit works properly. For inputs use **SW2**, **SW1** and **SW0** as **a**, **b**, and **c** respectively. For output **F**, use **LEDG1**


Experimental Results

Table:


a	b	c	Minterm	Maxterm	F
0	0	0	$a'b'c'$	$a+b+c$	1
0	0	1	$a'b'c$	$a+b+c'$	1
0	1	0	$a'bc'$	$a+b'+c$	0
0	1	1	$a'bc$	$a+b'+c'$	1
1	0	0	$ab'c'$	$a'+b+c$	1
1	0	1	$ab'c$	$a'+b+c'$	0
1	1	0	abc'	$a'+b'+c$	0
1	1	1	abc	$a'+b'+c'$	0

a) Minterm expansion: $a'b'c' + a'b'c + a'bc + ab'c'$

Circuit Design

 

Simulation

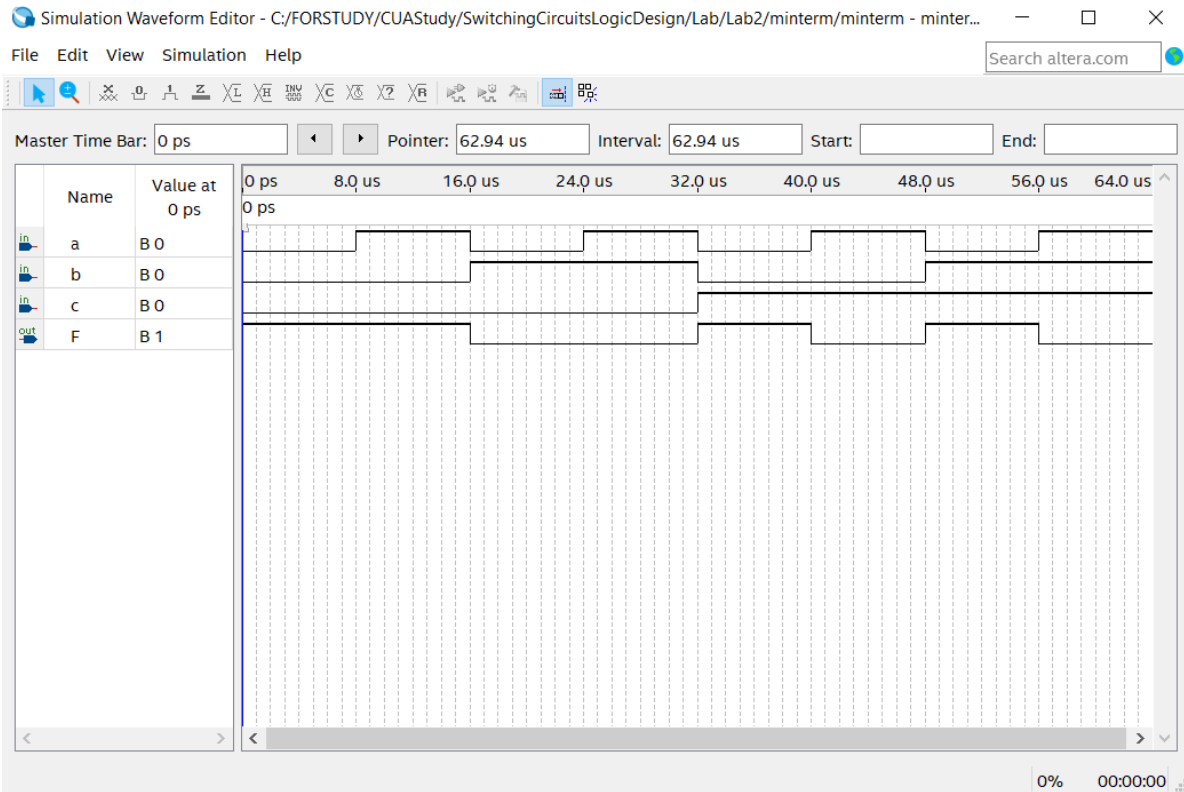

Pin planner

File Edit View Processing Tools Window Help

Search altera.com

Report

Report not available

Groups Report

Tasks

- Early Pin Planning
- Early Pin Planning...
- Run I/O Assignment...

Top View - Wire Bond
Cyclone IV E - EP4CE115F29C7

PIN_M14 (GND)

Pin Legend

Symbol	Pin Type
○	User I/O
●	User assign...
●	Fitter assign...
○	Unbonded ...
●	Reserved pin
○	Other confi...
○	DEV_OE
○	DEV_CLR
○	DIFF_n
○	DIFF_p
○	DQ

Named: * Edit: X

Filter: Pins: all


Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard
a	Input	PIN_AC27	5	B5_N2	PIN_AC27	2.5 V
b	Input	PIN_AC28	5	B5_N2	PIN_AC28	2.5 V
c	Input	PIN_AB28	5	B5_N1	PIN_AB28	2.5 V
F	Output	PIN_E22	7	B7_N0	PIN_E22	2.5 V
<<new node>>						

All Pins


0% 00:00:00

c) Maxterm expansion: $(a+b'+c)(a'+b+c')(a'+b'+c)(a'+b'+c')$

Circuit Design

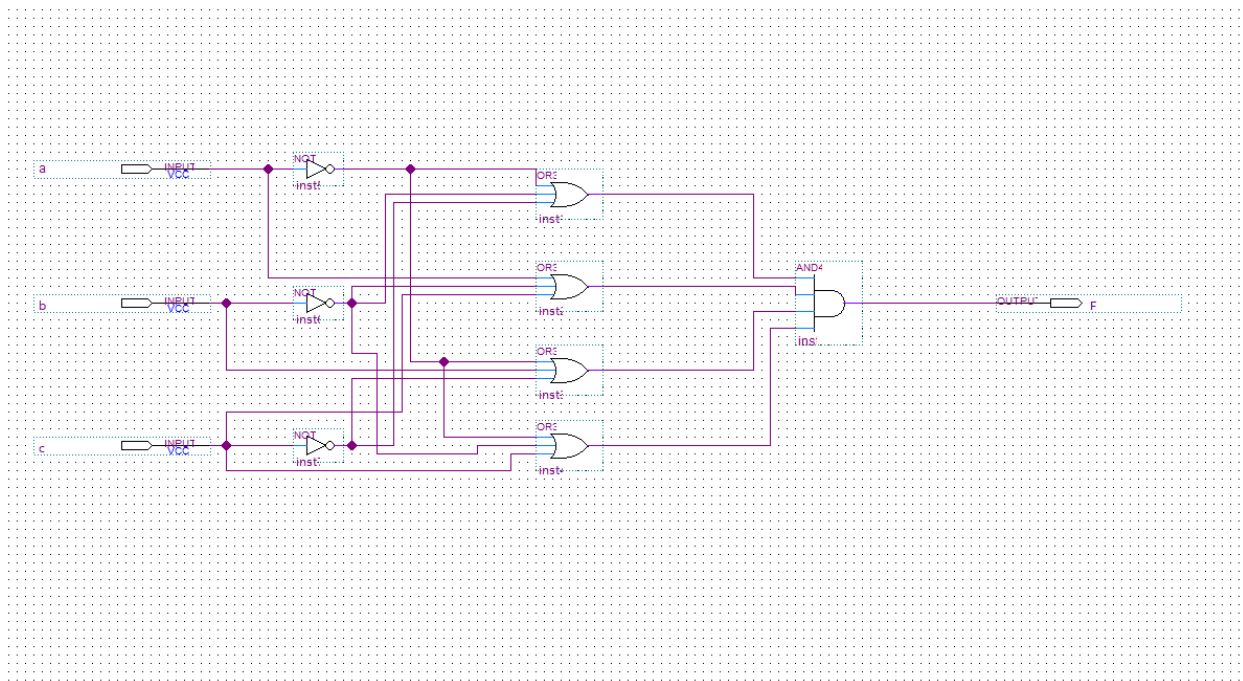

Simulation

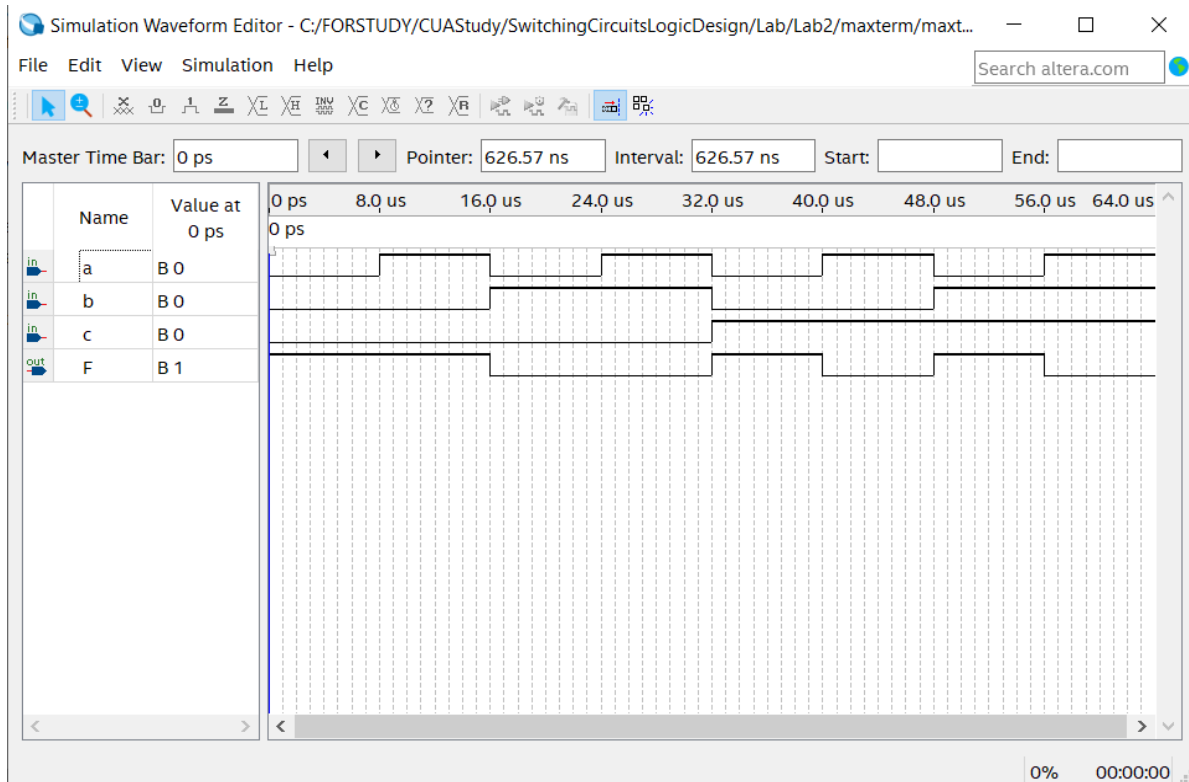

Pin planner

Report not available

Top View - Wire Bond
Cyclone IV E - EP4CE115F29C7

PIN_M14 (GND)

Pin Legend

Symbol	Pin Type
○	User I/O
●	User assign...
●	Fitter assign...
●	Unbonded ...
●	Reserved pin
○	Other confi...
E	DEV_OE
R	DEV_CLR
n	DIFF_n
p	DIFF_p
Q	DQ

Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard
in a	Input	PIN_AC27	5	B5_N2	PIN_AC27	2.5 V
in b	Input	PIN_AC28	5	B5_N2	PIN_AC28	2.5 V
in c	Input	PIN_AB28	5	B5_N1	PIN_AB28	2.5 V
out F	Output	PIN_E22	7	B7_N0	PIN_E22	2.5 V
<<new node>>						


0% 00:00:00

e) We have $a'b'c' + a'b'c + a'bc + ab'c'$


$$\Leftrightarrow b'c'(a+a') + a'c(b'+b)$$

$$\Leftrightarrow a'c + b'c'$$

Circuit Design

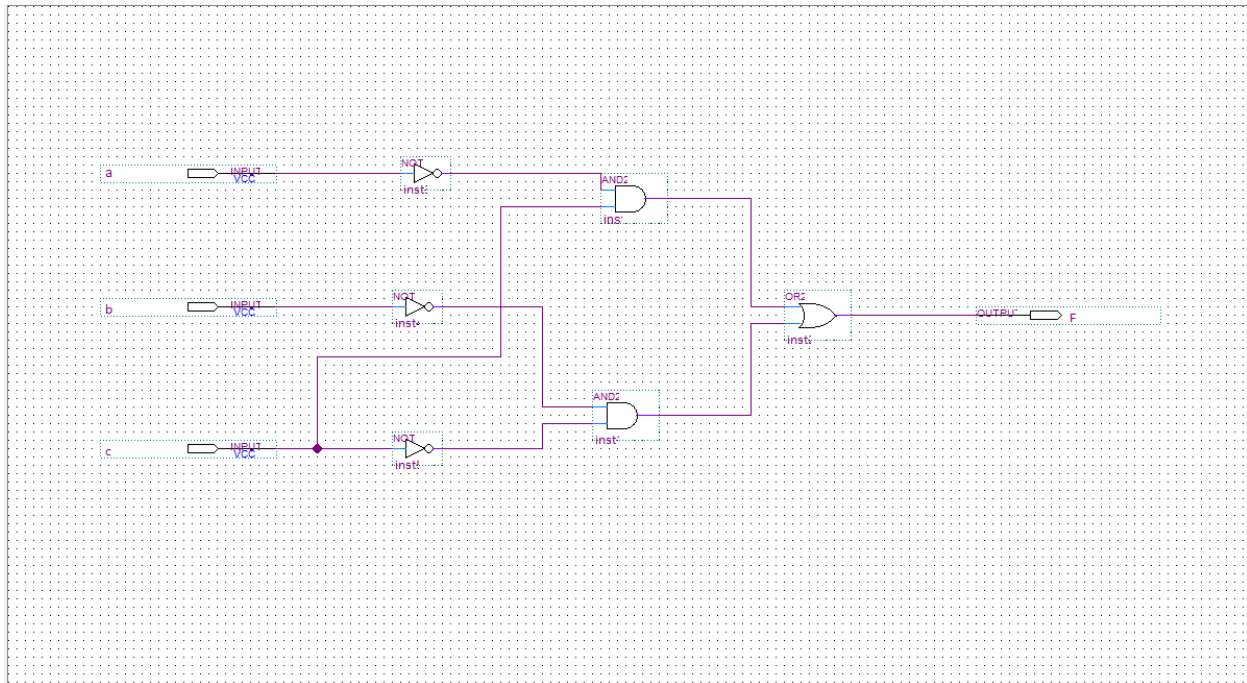

Simulation

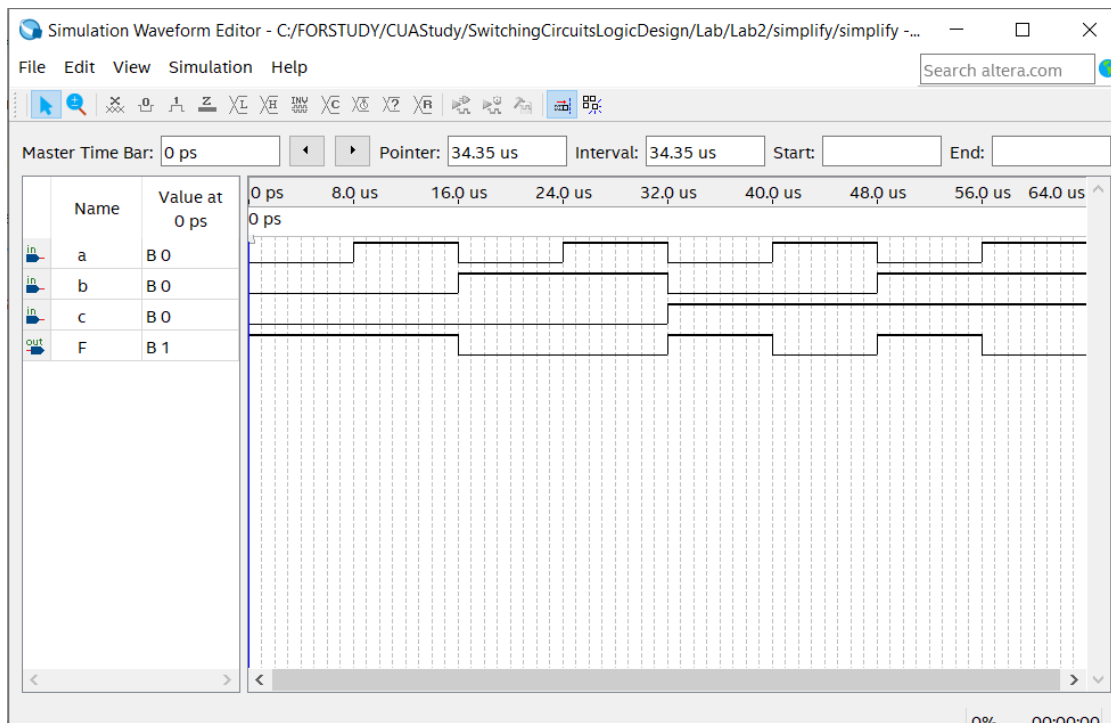

File Edit View Processing Tools Window Help

Search altera.com

Report

Report not available

Groups Report

Tasks

Early Pin Planning

Early Pin Planning...

Run I/O Assignment...

Top View - Wire Bond

Cyclone IV E - EP4CE116F29C7

PIN_M14 (GND)

Pin Legend

Symbol	Pin Type
○	User I/O
●	User assign...
●	Fitter assign...
○	Unbonded ...
●	Reserved pin
○	Other confi...
○	DEV_OE
○	DEV_CLR
○	DIFF_n
○	DIFF_p
○	DQ

Named: * Edit: X

Filter: Pins: all

Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard
in a	Input	PIN_AC27	5	B5_N2	PIN_AC27	2.5 V
in b	Input	PIN_AC28	5	B5_N2	PIN_AC28	2.5 V
in c	Input	PIN_AB28	5	B5_N1	PIN_AB28	2.5 V
out F	Output	PIN_E22	7	B7_N0	PIN_E22	2.5 V
<<new node>>						

0% 00:00:00

Conclusion

I learned how to find minterm and maxterm based on truth table. In addition, I learned how to simplify minterm and draw circuits base on minterm and maxterm of truth table.